

A Level Physics

18th Jan 2021 – Electrical Resistance Practical

Suitable for ALL exam boards



This session will look at a practical where potential difference (voltage) is changed, the current changes and the resistance of that component can be investigated.

Don't forget to **subscribe** on **YouTube** and turn on **notification** to be reminded about the **weekly livestreams** to support you as you prepare for any exams.

Question taken from:

Edexcel IAL Physics - January 2017 - Paper 3 (WPH03) - Question 8

- 8 A student investigates the resistance of a circuit component at different potential differences. Her results are shown in the table.

Potential difference across component V/V	Current through component I/mA
0	0
0.5	0
1.0	12
1.5	30
2	52
2.5	78

- (a) Criticise her results.

(3)

- (b) Plot a graph of V on the x -axis against I on the y -axis on the grid opposite and draw a line of best fit.

(5)

- (c) (i) Use your graph to determine the resistance at 40 mA.

(4)

Resistance =

- (ii) With reference to the resistance of the component, explain the shape of the graph between 0 and 0.5 V.

(2)



